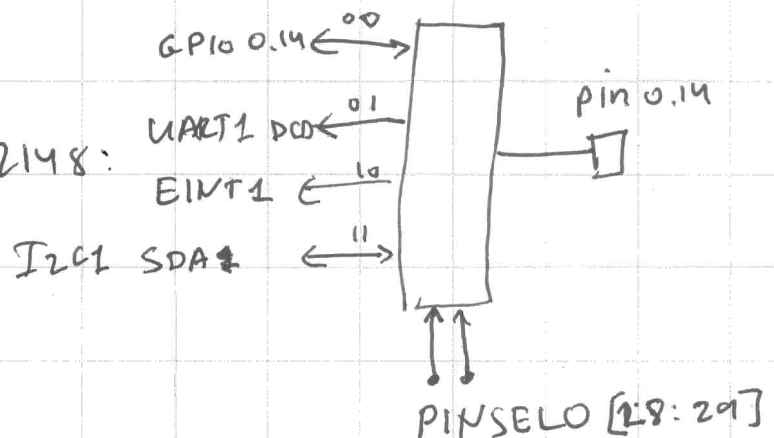


## Pin Selection

Pins are a precious resource: there are usually not enough pins for all the functions of all the peripherals.

- E.g. pin 0.14 on LPC2148:

4 functions for all pins of port 0, but only 2 functions for pins of port 1



- On MSP430, two functions for each pin (one is always GPIO), using PxSEL


- But: Enabling the DAC (digital-to-analog converter) connects it to the pin, independently of PxSEL (on MSP430F1611)

Not uncommon to have such irregularities, especially for ~~the~~ analog peripherals.


- Sometimes correct peripheral behavior depends on correct direction setting (input or output), sometimes this is automatic.

# Advanced Digital I/O (GPIO)

review of simple GPIO applications:

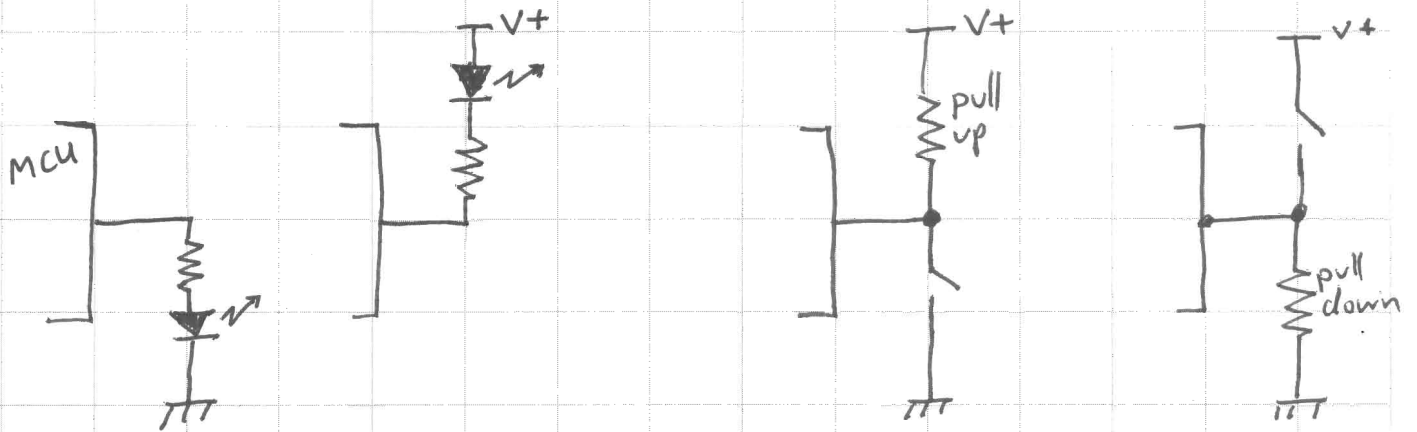


Structure of GPIO pin:

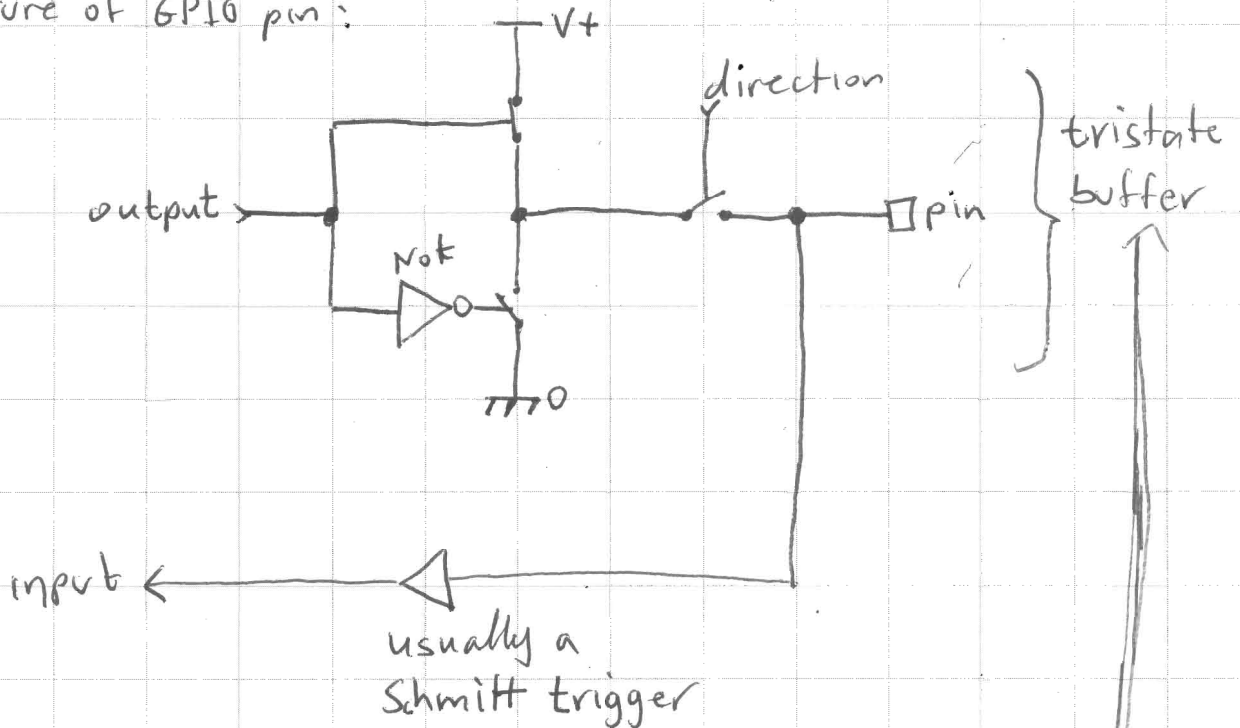


enable

States: high (H,  $V+$ , '1')  
low (L, 0V, '0')  
high-Z (disconnected)

## output characteristics of LPC 2148

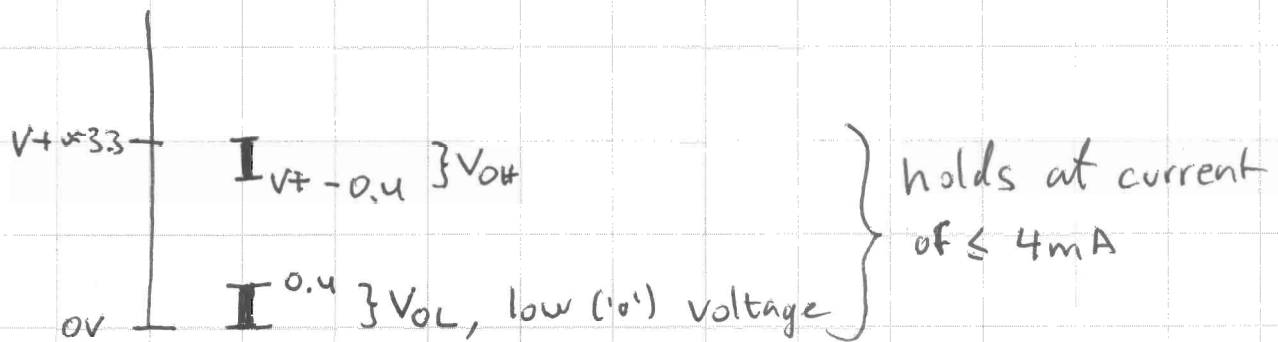


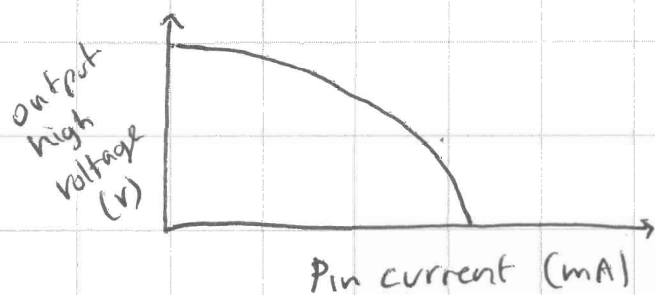When the pin sources (or sinks) more ~~more~~ current, output voltage drops (rises):



$\Rightarrow$  if a load (like an LED, a motor, etc) requires a lot of current or ~~run~~ runs on voltage  $\gg V+$ , we need an off-chip switch (amplifier).


## output Switches

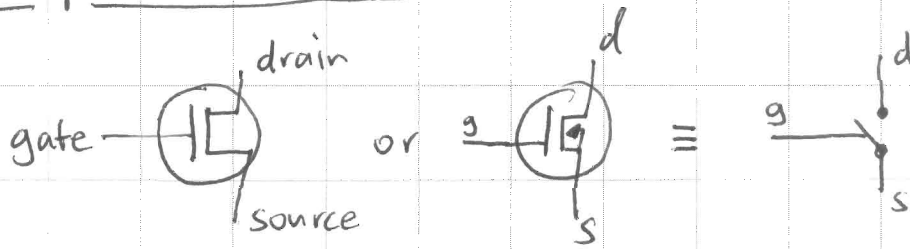

N-channel mosfet. Rule:  $V_g > V_s + \text{threshold}_{on} \Rightarrow \text{closed}$

$V_d - V_s$  can be <sup>much</sup> higher than thresholds.  $V_g \approx V_s + \text{threshold}_{off} \Rightarrow \text{open}$

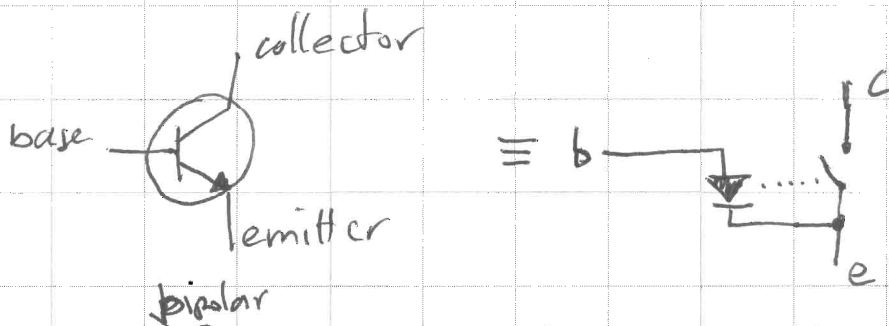can also be used in linear mode, not just as a switch



NPN <sup>bipolar</sup> transistor. Rule  $I_{be} > \text{threshold} \Rightarrow \text{closed}$






$I_{be} \approx 0 \Rightarrow \text{open}$

Again  $V_c$  can be very high.

can also be used as a linear amplifier

Because B-E junction is a diode  $V_{be} \approx 0.7V$

Using an off-chip switch:

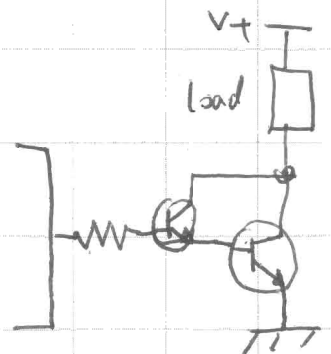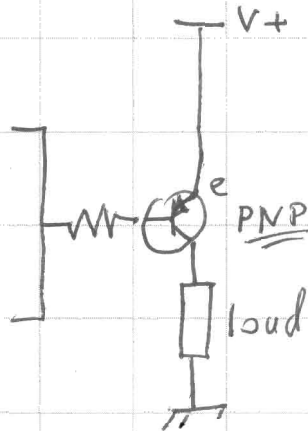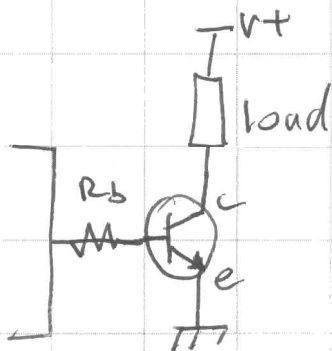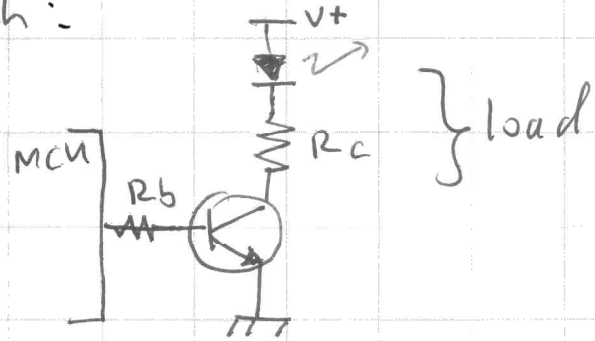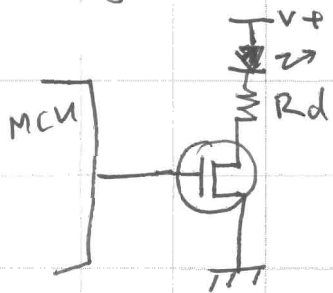


floating load



grounded load,  
~~more difficult~~  
~~more difficult~~  
~~more difficult~~  
 (more difficult  
~~more difficult~~  
~~more difficult~~  
 if  $V+$   
 is high)

Darlington  
 (higher load  
 current at  
 lower pin  
 current;  
 our rule hid  
 some  
 details...)

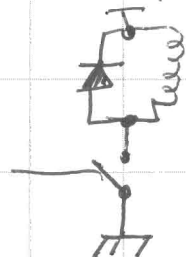
Inductive loads (relays, motors) require a flyback diode,  
 otherwise a high voltage develops ~~across~~ across  
 the switch when  
 the switch opens



# Master-Slave bus with tristate outputs

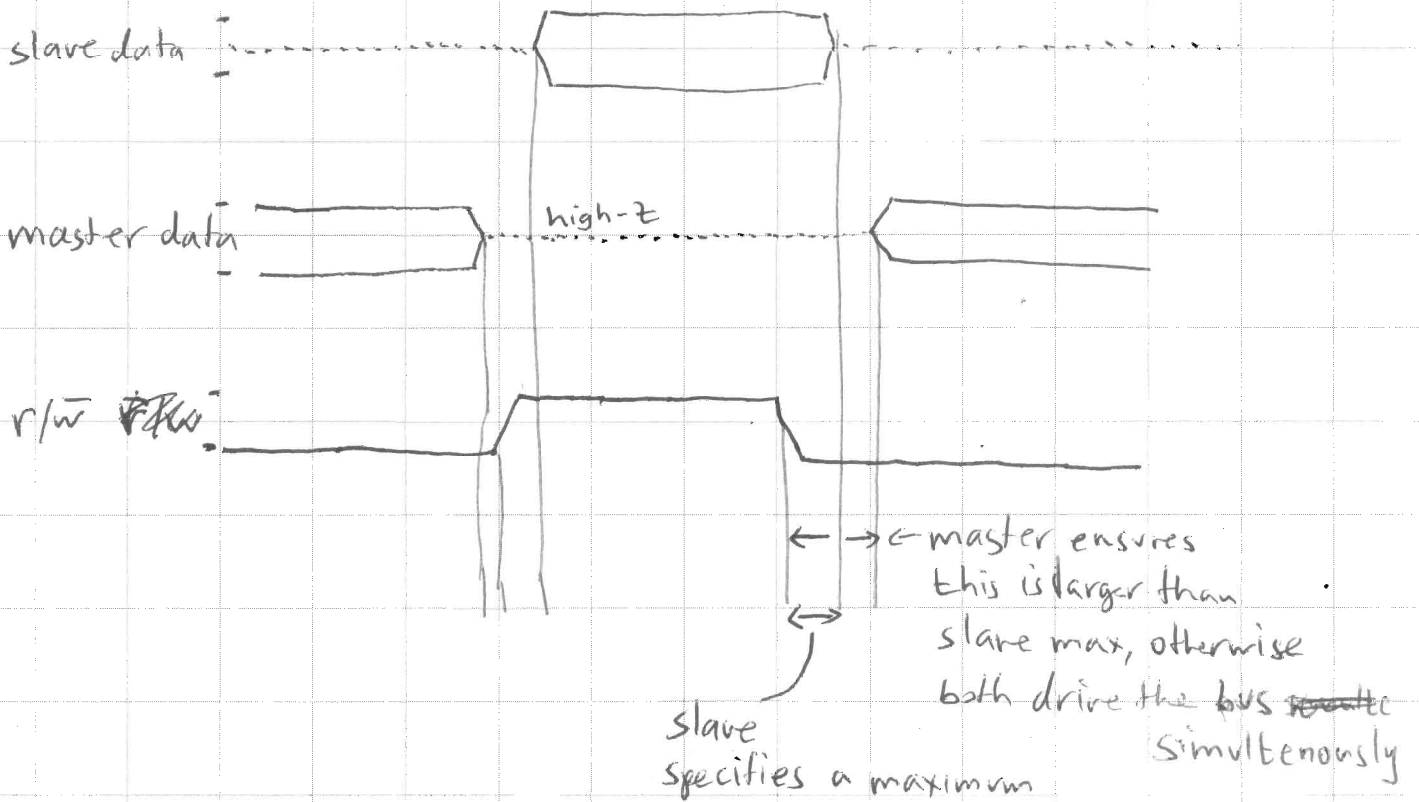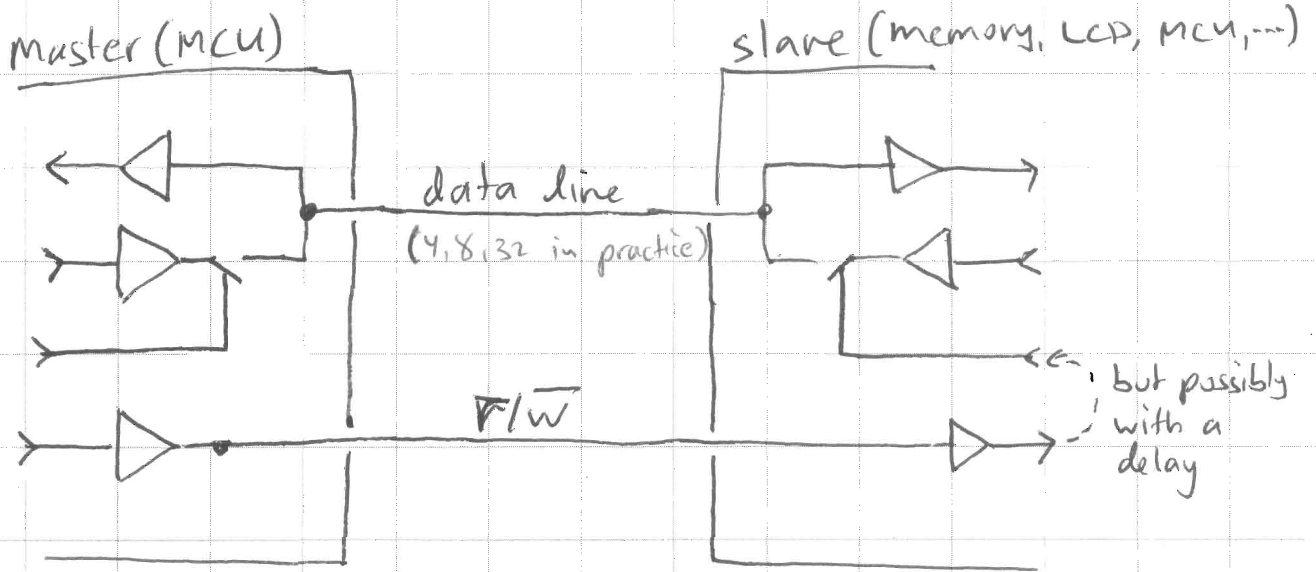

# Recessive-Dominant bus with open-drain outputs:

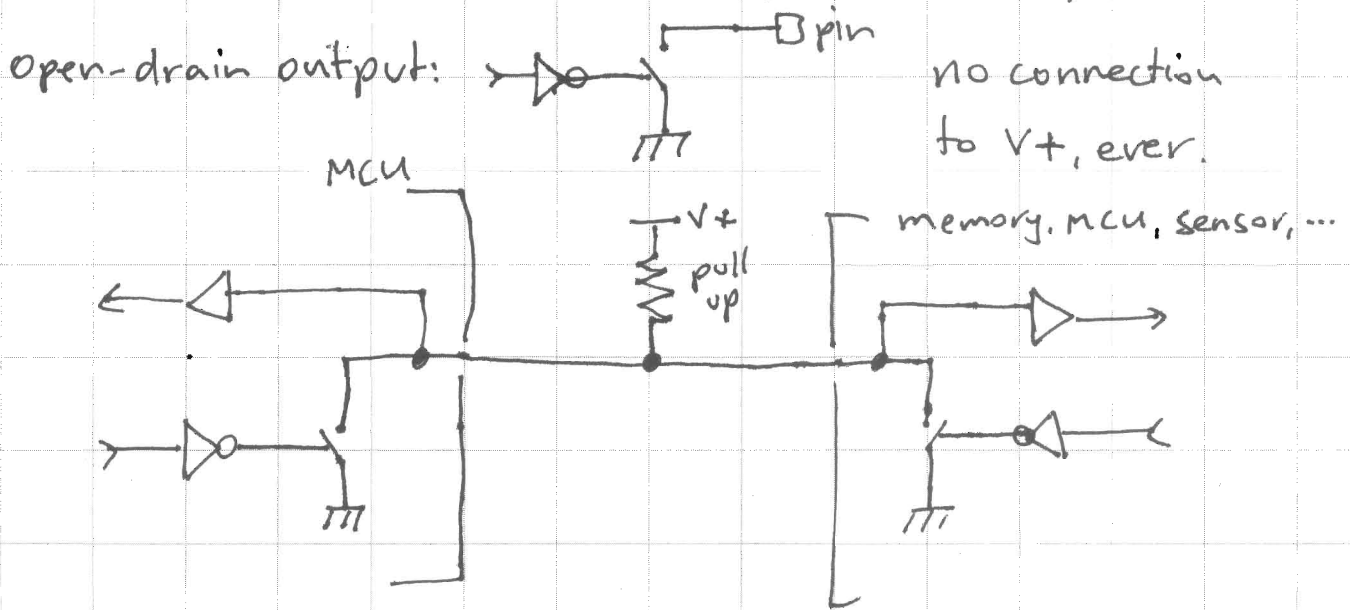

MCU 1  
O-D output

MCU 2  
O-D output

bus state

"wired nor"


- recessive  
- dominant

- Slower & shorter distances than tristate buses
- Other recessive-dominant signaling (e.g. differential in CAN)
- read-while you write (read a dominant when transmitting recessive ~~can be~~ used for arbitration in I<sup>2</sup>C, CAN)
- can sometimes simulate with tristate by switching enabled-low high  $\uparrow$   $\downarrow$   $\neq$


## Other advanced digital I/O behaviors

- External interrupts (edge or level)
- Internal pull-ups / pull-downs (newer MSP430s)
- ~~switching~~ configurable as open-drain or tristate  
(on LPC2148, I<sup>2</sup>C pins are opendrain, all others tristate)

- GPIO expanders:

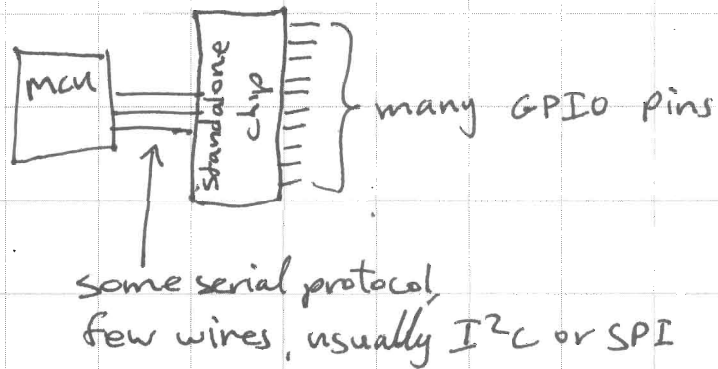


- Keyboard scanning

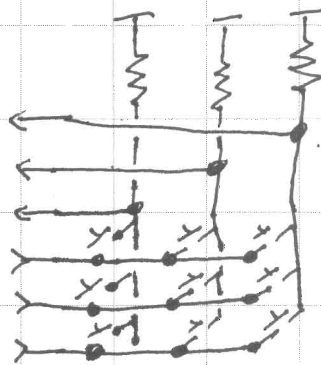

- output scanning

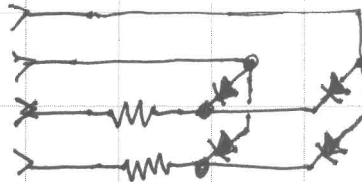columns may sink a lot  
of current, may require  
a transistor ~~switch~~  
switch.



make sure  
1 ~~resistor~~ LED  
per resistor,  
for consistent  
illumination